

CS220 Assignment-4

1) 3 bit gray code Counter

Gray code Counter is a type of counter in which at a time, only one binary digit changes its value.

Clock is acting as the input signal according to which states will change.

State Assignment

Digit	Gray Code	Assigned State
0	000	S0
1	001	S1
2	011	S2
3	010	S3
4	110	S4
5	111	S5
6	101	S6
7	100	S7

State Table

Present State			Next state		
Q2	Q1	Q0	Q2	Q1	Q0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1

1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

Excitation and Output Table

Present State			Next State			Flip Flop Excitations			Output
Q2	Q1	Q0	Q2'	Q1'	Q0'	D2	D1	D0	Z
0	0	0	0	0	1	0	0	1	0
0	0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	0	0	1	0
0	1	0	1	1	0	1	0	0	0
1	1	0	1	1	1	0	0	1	0
1	1	1	1	0	1	0	1	0	0
1	0	1	1	0	0	0	0	1	0
1	0	0	0	0	0	1	0	0	1

- K maps

D0

$$D_0 = \overline{Q_2} \oplus Q_1 \oplus Q_0$$

D1

		g_1, g_0			
		00	01	11	10
g_2	0	0	1	0	0
	1	0	0	1	0

$$D_1 = \overline{g_2} \overline{g_1} g_0 + g_2 g_1 g_0$$

D2

		g_1, g_0			
		00	01	11	10
g_2	0	0	0	0	1
	1	1	0	0	0


$$D_2 = g_2 \overline{g_1} \overline{g_0} + \overline{g_2} g_1 \overline{g_0}$$


Z(output)

		g_1, g_0			
		00	01	11	10
g_2	0	0	0	0	0
	1	1	0	0	0

$$Z = g_2 \overline{g_1} \overline{g_0}$$

Circuit Diagram

 

 

2)

Eight-bit adder/subtractor

To add/subtract two eight-bit two's complement numbers

Verilog Implementation

It is implemented in two modules. First, the module implements a one-bit adder/subtractor with four inputs a , b , cin , and $opcode$, and two outputs sum and $carry$.

For the addition operation the input $opcode$ will be 0 and 1 for subtraction operation.

For $opcode$ as 1, we take 2's complement of b as

$$b = \sim b + 8'b00000001$$

Which is implemented as the addition of 1 in last bit by making initial carry input 1 and taking bit wise negation of b

Otherwise, carry input initially is 0 and b is same as input

Then we take sum bitwise and also take carry out 1 when we have any two of $a, b, carry_in$ or all are 1.

These bitwise sum and carry outputs are stored in 8-bit wire outputs using the "for loop" to call 1-bit adder/subtractor `"oneBit_Adder(input a, input b, input cin, input opcode, output sum, output cout);"` within the module

`"eightBit_adder(a,b,cin,opcode,sum,cout,overflow);"` keeps on storing the bits of sum so obtained.. The last carry out is stored in "cout" as given as final output to display.

Also we assign the overflow whenever the last and second last carry in is the same.

Truth Table of one bit adder/subtractor

Inputs				Outputs	
A	B	Carry in	Op code	sum	cout
0	0	0	0	0	0
		1		1	0
		0	1	1	0
		1		0	1
0	1	0	0	1	0
		1		0	1
		0	1	0	0
		1		1	0
1	1	0	0	0	1
		1		1	1
		0	1	1	0
		1		0	1
1	0	0	0	1	0
		1		0	1
		0	1	0	1
		1		1	1