

# CS220 Assignment 3

## 1. Sequence Detector (1010):

A sequential detector is a sequential state machine that takes an input string of bits and generates an output 1 whenever the target sequence (1010) is detected. It is implemented by constructing a Finite State Machine (FSM) which allows for overlapping too, i.e, the last bit of one sequence becomes first bit of the next sequence.

We are implementing it through a Mealy machine.

In a Mealy machine, output depends on the present state as well as the external input (X).


FSM construction of Sequence Detector :

- The FSM is implemented using three always blocks, one block for changing the state on getting input ( combinational logic ), one for changing the current state whenever the clock (clk) has positive edge (sequential logic) and one for giving output ( output logic).
- Four states are defined, IDLE, state1, state2, and state3.

```
parameter IDLE = 2'b00, //initially
state1 = 2'b01, //state when it gets 10 from idle state
state2= 2'b10, //state when it gets 101
state3= 2'b11; //state when it gets 1010
```

- Initially, the clock is set 0 and reset is also set 0. Then 8-bit input is given which sends one-bit to the module seq\_detector each time the edge becomes positive in the clock.
- Initially, the state is defined as IDLE and depending upon the input the next state is determined.
- As the state changes, an one-bit output is given. If sequence 1010 gets detected, output is given as 1 else 0.
- Again, when posedge arrives, the next 1-bit input is send, the state changes and the sequence is determined.

❖ State Diagram :

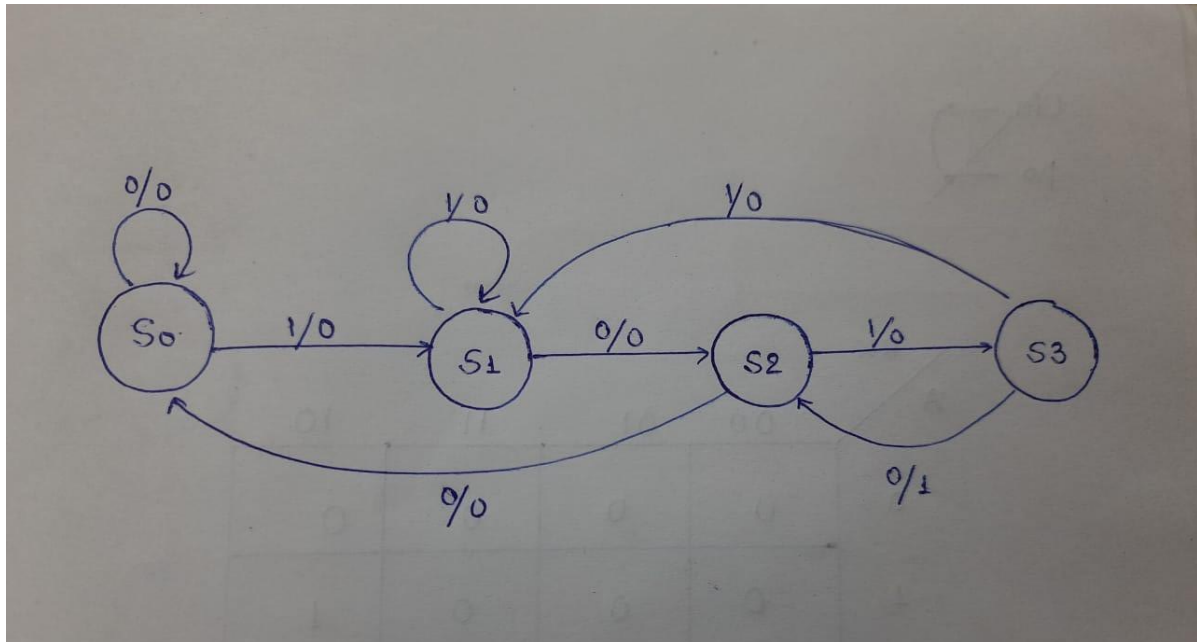

Here S0 is IDLE as stated above.

❖ Output Table :

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
00	00	01	0	0
01	10	01	0	0
10	00	11	0	0
11	10	11	1	0

❖ Excitation Table :

Present State		Input	Next State		Flip-flop excitations		Output
A	B	X	A'	B'	Da	Db	Z
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0

0	1	1	0	1	0	1	0
1	0	0	0	0	0	0	0
1	0	1	1	1	1	1	0
1	1	0	1	0	1	0	1
1	1	1	1	1	1	1	0

❖ K-map

		00	01	11	10
A \ Bx	0	0	0	0	1
	1	0	1	1	1

∴  $D_a = Ax + B\bar{x}$



BX		00	01	11	10
A	0	0	1	1	0
	1	0	1	1	0

$D_b = X$

BX		00	01	11	10
A	0	0	0	0	0
	1	0	0	0	1

$Z = AB\overline{X}$

❖ Circuit / Logic Diagram

  

#### ❖ Verilog Code

```
module seq_detector(clk, reset, in, out);
    input clk, reset, in;
    output out;
```

```

wire clk,reset;
wire in; //1-bit input
reg out; //1-bit output
parameter SIZE = 2; //setting parameter SIZE as 2

//setting parameters as different states
parameter IDLE = 2'b00, //initially
state1 = 2'b01, //state when it gets 10 from idle state
state2= 2'b10, //state when it gets 101
state3= 2'b11; //state when it gets 1010

reg [SIZE-1:0] state; //current state
reg [SIZE-1:0] next_state; //next state
initial begin
    state = IDLE;
end

always @(state or in) begin
    next_state= IDLE;
    case (state)

        //when it gets input after it is at IDLE state
        IDLE: if (~in) begin

            next_state= IDLE;
        end
        else begin
            next_state = state1;
        end

        //when it gets input after it is at state1
        state1: if(~in) begin

            next_state = state2;
        end
        else begin
            next_state= state1;
        end
    endcase
end

```

```

        end

        //when it gets input after it is at state2
        state2: if(~in) begin

            next_state = IDLE;
        end
        else begin
            next_state = state3;
        end

        //when it gets input after it is at state3
        state3: if(~in) begin
            next_state= state2;
        end
        else begin
            next_state = state1;
        end

        default: begin
            next_state = IDLE;
        end

    endcase

end

always @(posedge clk) begin

    if(reset == 1'b1) begin

        state = IDLE; //new (8-bit) input
    end
    else begin

        state = next_state; //continuation of the input
    end

end

```

```

always @(state or in) begin

    if(reset == 1'b1) begin
        out = 1'b0;
    end

    else begin
        if(state == state3) begin
            if(in == 1'b0) begin
                out = 1'b1; //output when it finds the sequence of
1010
            end
            else begin
                out = 1'b0; ////output when it is at any other state
            end
        end
        else begin
            out = 1'b0;
        end
    end

end

endmodule

```

★ Testbench :

```

`include "A3_Q1_seq_detector.v"

module seq_tb();

reg clk, reset, inp;
reg [7:0] in; //reg to store 7-bit input
reg [7:0] out; //reg to store 7-bit output
wire outp; //to store 1-bit after each 1-bit input

```



```

integer i;

always #2 clk=~clk; //oscillation in clock

seq_detector x(clk,reset,inp,outp);

initial begin
    clk= 1'b0; //setting clock to 0 initially
    reset = 1'b0; //setting reset to 0 initially and after each input
case changing to 1 to get again IDLE state
    in = 8'b10101010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01110110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01010010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b10100010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01011010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01010110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b00010010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b00010110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b11001010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01110011; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;

```

```

#5 reset =1'b0;
in = 8'b01110100; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b11010010; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b01010110; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b00010010; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b01010000; #35 $display("input = %b output= %b",in,out);

#5 $finish;

end

//giving input bit-wise whenever the 7-bit input changes
always @(in) begin
    for(i=7;i>=0;i-=1) begin
        #2
        inp= in[i];
        #2
        out[i]= outp;
    end
end

endmodule

```

### **3-bit odd parity bit generator:**

A 3-bit odd parity bit generator takes 3 bits input one by one and generates an output 1 if the number of 1s are even or 0 otherwise. It can be implemented by Finite State Machine (FSM) which keeps count as states. It is a type of Moore Machine which gives output on the basis of Current State .

FSM Construction of 3-bit odd parity generator :

- The FSM is implemented using three always blocks, one block for changing the state on getting input ( combinational logic ), one for changing the current state whenever the clock (clk) has positive edge (sequential logic) and one for giving output ( output logic).
- 11 states are defined, IDLE, odd0\_even0, odd0\_even1, odd1\_even0, odd0\_even2, odd1\_even1, odd2\_even0, odd2\_even1, odd1\_even2, odd3\_even0, odd3\_even1

- We are defining the states on the basis of number of 0 and 1 we encounter, for eg odd2\_even1 means 2 bits are 1(odd) and 1 bit is 0(even)
- .

States :

```

• IDLE = 4'b0000,
• odd0_even0 = 4'b1000,
• odd0_even1 = 4'b0010,
• odd1_even0 = 4'b0001,
• odd0_even2 = 4'b0110,
• odd1_even1 = 4'b0011,
• odd2_even0 = 4'b0101,
• odd0_even3 = 4'b1110,
• odd1_even2 = 4'b0111,
• odd2_even1 = 4'b1011,
• odd3_even0 = 4'b1101;

```

- Initially, the clock is set 0 and reset is also set 0. Then 3-bit input is given which sends one-bit to the module parity\_gen each time the edge becomes positive in the clock.
- Initially, the state is defined as IDLE and depending upon the input the next state is determined.
- The input changes each time the edge becomes positive in the clock and at the end of the 3-bit input, output is given as 1 in case the number of 1's in the sequence is even, 0 in other case.

Truth Table:-

Inputs (3-bits)			Output
A	B	C	O
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1


1	1	1	0
---	---	---	---

K-Map

		BC			
		00	01	11	10
A	0	1	0	1	0
	1	0	1	0	1

$$\begin{aligned}\text{Output} &= A'B'C' + AB'C + A'BC + ABC' \\ &= A \oplus (B \oplus C)'\end{aligned}$$

Logic Circuit:

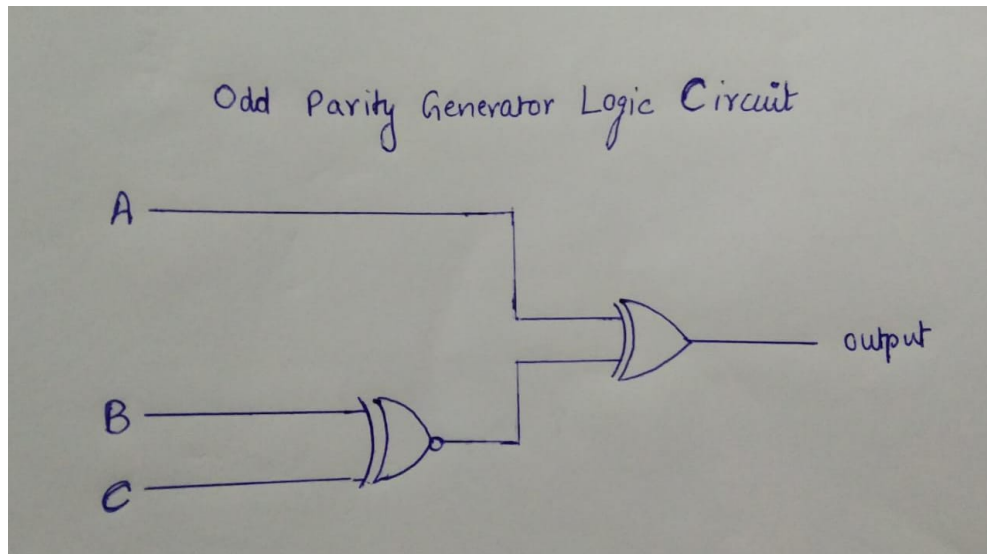


Excitation Table:

For any input with new (8-bit)input the state changes to IDLE\_ state

Previous State	Next State	Input	Output
0000	1000	0/1	0
1000	0001	1	0
1000	0010	0	0

0010	0110	0	0
0010	0011	1	0
0001	0011	0	0
0001	0101	1	0
0110	1110	0	0
0110	0111	1	0
0011	0111	0	0
0011	1011	1	0
0101	1011	0	0
0101	1101	1	0
1110	0000	0/1	1
0111	0000	0/1	0
1011	0000	0/1	1
1101	0000	0/1	0

State diagram:

 

Moore state diagram of 3 bit parity generator

Verilog code:

```

module parity_gen(clk,reset,in,out);

input clk,reset,in;
output out;

wire clk,reset;
wire in; //1-bit input
reg out; //1-bit output
parameter SIZE = 4; //setting parameter SIZE as 4

//setting parameters as different states
parameter IDLE = 4'b0000, //initial state
odd0_even0 = 4'b1000, //state when there are zero 1s and zero 0s
odd0_even1 = 4'b0010, //state when there are zero 1s and one 0s
odd1_even0 = 4'b0001, //state when there are one 1s and zero 0s
odd0_even2 = 4'b0110, //state when there are zero 1s and two 0s

```

```

odd1_even1 = 4'b0011, //state when there are one 1s and one 0s
odd2_even0 = 4'b0101, //state when there are two 1s and zero 0s
odd0_even3 = 4'b1110, //state when there are zero 1s and three 0s
odd1_even2 = 4'b0111, //state when there are one 1s and two 0s
odd2_even1 = 4'b1011, //state when there are two 1s and one 0s
odd3_even0 = 4'b1101; //state when there are three 1s and zero 0s

reg [SIZE-1:0] state; //current state
reg [SIZE-1:0] next_state; //next state
initial begin
    state = IDLE;
end

always @(state or in) begin

    next_state= IDLE;
    case (state)
        IDLE: next_state= odd0_even0;

        //when it gets input after it is at odd0_even0 state
        odd0_even0 :if (in) begin
            next_state= odd1_even0;
        end
        else begin
            next_state= odd0_even1;
        end

        //when it gets input after it is at odd0_even1 state
        odd0_even1 : if (in) begin
            next_state= odd1_even1;
        end
        else begin
            next_state= odd0_even2;
        end

        //when it gets input after it is at odd1_even0 state
        odd1_even0: if(in) begin
            next_state= odd2_even0;
        end
    end
end

```



```
else begin
    next_state= odd1_even1;
end

//when it gets input after it is at odd0_even2 state
odd0_even2: if(in) begin
    next_state= odd1_even2;
end
else begin
    next_state= odd0_even3;
end

//when it gets input after it is at odd1_even1 state
odd1_even1: if(in) begin
    next_state= odd2_even1;
end
else begin
    next_state= odd1_even2;
end

//when it gets input after it is at odd2_even0 state
odd2_even0: if(in) begin
    next_state= odd3_even0;
end
else begin
    next_state= odd2_even1;
end

//when it gets input after it is at odd0_even3 state
odd0_even3: if(in) begin
    next_state= IDLE;
end
else begin
    next_state= IDLE;
end

//when it gets input after it is at odd1_even2 state
odd1_even2: if(in) begin
    next_state= IDLE;
end
```

```

        else begin
            next_state= IDLE;
        end

        //when it gets input after it is at odd2_even1 state
        odd2_even1: if(in) begin
            next_state= IDLE;
        end
        else begin
            next_state= IDLE;
        end

        //when it gets input after it is at odd3_even0 state
        odd3_even0: if(in) begin
            next_state= IDLE;
        end
        else begin
            next_state= IDLE;
        end
        default: next_state = IDLE;
    endcase
end

always @(posedge clk ) begin
    if(reset) begin
        state = #1 IDLE; //new (3-bit) input
    end
    else begin
        state = #1 next_state; //continuation of the input
    end
end

always @(in or state ) begin
    //output when it is at state with odd number of ones
    if(state == odd2_even1) begin
        out = #1 1'b1;
    end
    else if(state == odd0_even3) begin
        out = #1 1'b1;
    end
end

```

```

    end
    else begin
        out = #1 1'b0; //otherwise condition
    end
end

end

endmodule

```

Testbench:

```

`include "A3_Q2_parity_gen.v"

module tstbnch();

reg clk,reset,inp,out;
reg [2:0] in; //input register
wire outp; //output wire
integer i;

always #1 clk = ~clk; //for clock oscillation

parity_gen x(clk,reset,inp,outp);

initial begin
    clk = 1'b0; //setting clock to 0 initially
    reset = 1'b0; //setting reset to 0 initially and after each input case
    changing to 1 to get again IDLE state
    in = 3'b000;
    #10
    $display("input=%b parity_bit=%b",in,outp);
    reset=1'b1;
    #5 reset=1'b0;
    in = 3'b001;
    #10
    $display("input=%b parity_bit=%b",in,outp);
    reset=1'b1;

```

```
#5 reset=1'b0;
in = 3'b010;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b011;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b100;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b101;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b110;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b111;
#10
$display("input=%b parity_bit=%b",in, outp);
```

```
#3$finish;
```

```
end
```

```
//giving input bit-wise whenever the 3-bit input changes
```

```
always @(in) begin
```

```
    for(i=0;i<3;i+=1) begin
```

```
        #2
```

```
        inp= in[i];
```

```
    end
```

```
end
```

```
always @(outp) begin
```

```
    // $display("outpchange %d",$time);
```

```
end
```

```
endmodule
```